

# GATE 2022 33.BM

EE23BTECH11012 - Chavan Dinesh\*

**Question:** A series  $RLC$  circuit with  $R = 10\Omega$ ,  $L = 50mH$  and  $C = 100\mu F$  connected to 200 V, 50 Hz supply consumes power  $P$ . The value of  $L$  is changed such that this circuit consumes same power  $P$  but operates with lagging power factor. The new value of  $L$  is \_\_\_\_\_  $mH$  (rounded off to two decimal places). (GATE 33 BM 2022)

**Solution:**

Parameter	Description	Value
$R$	Resistance	$10\Omega$
$C$	Capacitance	$100\mu F$
$L_{old}$	Inductor	$50mH$
$L_{new}$	New Inductor	
$Z_{old}$	Old Impedance	
$Z^*$	New Impedance	

TABLE 1


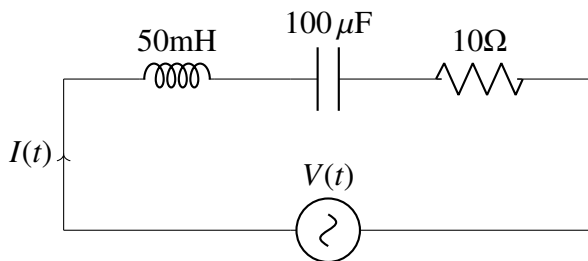


Fig. 1

From Fig. 1

In  $s$  - domain,

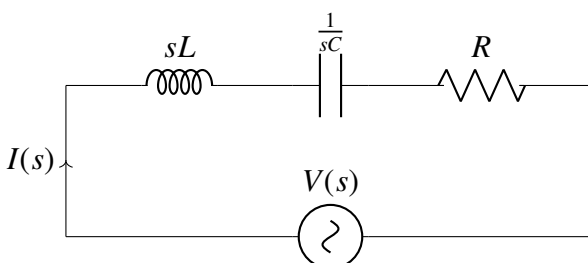

$$Z = R + sL_{old} + \frac{1}{sC} \quad (1)$$

As the circuit consumes same power  $P$  but operates with lagging power factor :  
The new impedance( $Z^*$ ) will be :

$$Z^* = R + sL_{new} + \frac{1}{sC} \quad (2)$$

Comparing the imaginary parts of the impedances:

$$sL_{old} + \frac{1}{sC} = -\left(sL_{new} + \frac{1}{sC}\right) \quad (3)$$

Taking  $s = j2\pi f$  :

$$j\left(2\pi f L_{old} - \frac{1}{2\pi f C}\right) = -j\left(2\pi f L_{new} - \frac{1}{2\pi f C}\right) \quad (4)$$

From Table 1:

$$L_{new} \approx 152.7mH \quad (5)$$